

Name of the Student Rahul AgarwalRoll No. 23112c1268**MAULANA AZAD NATIONAL INSTITUTE OF TECHNOLOGY**

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

MONTH &amp; YEAR: NOV 2024

**EXAMINATION: END TERM EXAM**

Branch: CSE

Course: B. Tech

Semester: III

Subject Code: CSE 214

Subject Name: Digital Electronics

Max Marks: 50

Time: 180 minutes


Note: Answer all Questions. Attempt all the parts of a Question in continuation.

Q. 1 (a) Check whether the given function  $f(A, B, C, D) = \sum m(1, 2, 15, 0, 6, 5, 4, 7)$  is an orthogonal function or not. If yes, then find the number of orthogonal functions? (5) CO1

(b) In a prime implicant chart representing a Boolean expression  $f(w, x, y, z)$ . Columns represent minterms and rows represent prime implicants. Identify P, Q, R, S, a, b. (5) CO2

	0	4	5	7	8	a	b
P	✓	✓					
Q	✓				✓		
R		✓	✓				
S			✓	✓		✓	✓

 
Q. 2 (a) Consider the following combinational circuit implemented using 3 to 8 decoder, 4 to 1 MUX and 2 to 1 MUX. Find the output F in standard sum of product (SOP) form. (5) CO3




(b) Consider a 100-bit parallel adder and subtractor circuit that is designed with the help of NOT, OR, AND, NAND and NOR gates only. The cost and time delay of each gate is 1 rupee and 1 time unit respectively. What will be the total time delay and total cost to implement the subtraction operation of two 100-bit numbers? Compare the delay and cost of this system with a 100-bit look-ahead carry subtractor circuit. (5) CO3

Q. 3 (a) Consider realization of **64 X 1** MUX from **4 X 1**. If input given at select lines is 100110. Find MUX number and its input line number at stage1 which is shown as output? (5) CO3

 
- (b) Consider the following sequential synchronous circuit with initial state  $Q_0 = Q_1 = Q_2 = 0$ . The state of the circuit is given by the equation  $4R + 2Q + P$ . What will be the counting sequence of the circuit? (5)CO4



 - Q. 4 (a) Consider the following CKT involving a positive edge triggered T F/F (initially zero). (5)




 Consider the following timing diagram. Find the timing diagram for output Y.



- (b) Construct 4 bit switch tail ring counter using T flip flop. (5)CO4

 - Q. 5 (a) Consider the following Asynchronous Ripple Counter using T F/Fs with initial State is 000. Find the counting sequences generated by Counter. (All the f/fs are negative edge triggered) (5)CO4



- (b) Consider a serial in Serial out register with initial state  $Q_0 = Q_1 = Q_2 = 0$ . The following data: 1011011 is supplied to the data terminal from LSB one bit per clock. What will be the content of shift register after 7<sup>th</sup> clock cycle? (5)CO4

